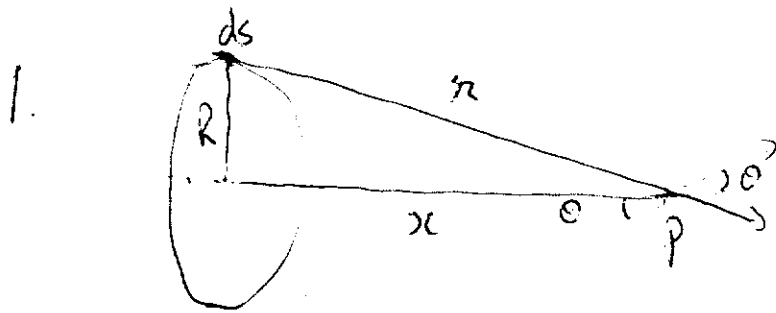


PHYSICS Part 2 Test solutions



(a) By symmetry the electric field at  $P$  will be in the  $x$  direction.

The field due to an element of charge  $dq = \lambda ds$  will be in the direction shown and will have a

value  $dE = \frac{dq}{4\pi\epsilon_0 r^2}$

The total field will then be  $\int \frac{dq \cos\theta}{4\pi\epsilon_0 r^2}$

$$= \frac{Q}{4\pi\epsilon_0 r^2} \cdot \frac{x}{r}$$

$$= \frac{Qx}{4\pi\epsilon_0 (x^2 + R^2)^{3/2}}$$

(b) If the point mass  $Q$  is at the centre of the ring, the system has a potential energy of

$$\frac{Q^2}{4\pi\epsilon_0 R}$$

This energy is converted to kinetic energy so  $\frac{1}{2} M v^2 = \frac{Q^2}{4\pi\epsilon_0 R}$

$$v = \sqrt{\frac{Q^2}{2\pi\epsilon_0 M R}}$$

2. (a) Capacitor A may be considered as two capacitors in parallel, one with dielectric and one without.

$$\begin{aligned}
 \text{Capacitance of A is then } C &= \frac{\epsilon \epsilon_0 A_1}{d} + \frac{\epsilon_0 A_2}{d} \\
 &= \frac{3 \times 9.85 \times 10^{-12} \times 2 \times 15 \times 10^{-4}}{0.5 \times 10^{-2}} + \frac{9.85 \times 10^{-12} \times 2 \times 0.5 \times 10^{-4}}{0.5 \times 10^{-2}} \\
 &= \frac{9.85 \times 10^{-12} \times 10^{-4}}{0.5 \times 10^{-2}} (9+1) \\
 &= 1.97 \times 10^{-12} \sim 2 \text{ pF.}
 \end{aligned}$$

(b) Total capacitance of two in series

$$\frac{1}{C_s} = \frac{1}{2} + \frac{1}{4} = \frac{3}{4} \quad \text{so } C_s = \frac{4}{3} \text{ pF.}$$

Charge on each capacitor  $Q = C_s V = \frac{4}{3} \times 12 = 16 \text{ pC}$

$$\text{P.D. across A is } V = \frac{Q}{C} = \frac{16 \times 10^{-12}}{2 \times 10^{-12}} = 8 \text{ V.}$$

(c) Capacitance of A will decrease and so will total capacitance of the circuit.

Thus stored energy  $= \frac{1}{2} C V^2$  will decrease.

Energy will be lost to heat as current flows around the circuit during the change.

$$3. (a) \quad R = \frac{\rho l}{A} = \frac{1.7 \times 10^{-8} \times 2}{\pi \left( \frac{1 \times 10^{-3}}{2} \right)^2} = 0.043 \text{ ohm.}$$


$$(b) \quad \Delta R = \frac{\rho \Delta l}{A} = \frac{1.7 \times 10^{-8} \times 1 \times 10^{-3}}{\pi \left( \frac{1 \times 10^{-3}}{2} \right)^2} = 2.16 \times 10^{-5} \text{ ohm.}$$

(c) Labelling currents as shown,

$$-5 - 2i_1 + 2i_2 + 4 = 0 \quad \dots (1)$$

$$-4 - 2i_2 + 2i_3 - 2 = 0 \quad \dots (2)$$

$$i_1 + i_2 + i_3 = 0 \quad \dots (3)$$

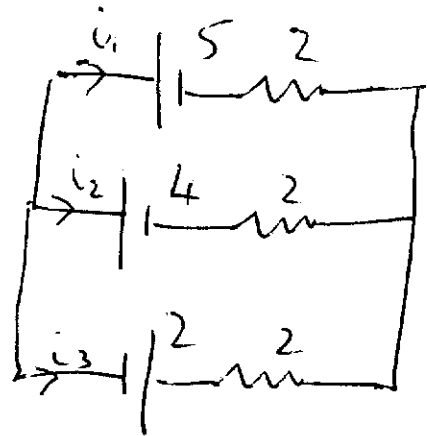

From (1) + (3):  $-5 + 2i_2 + 2i_3 + 2i_2 + 4 = 0$

$$\text{or } 4i_2 + 2i_3 - 1 = 0$$

as (2) is  $-2i_2 + 2i_3 - 6 = 0$

Substituting  $6i_2 + 5 = 0$

$$i_2 = -5/6 \text{ A.}$$

4. Force on ~~the~~ <sup>bottom</sup> part of wire is

$$F_{\text{BOT}} = B_4 i l = \frac{4 \times 10^{-7}}{4 \times 10^{-2}} \times 5 \times 0.1$$
$$= 5 \times 10^{-6} \text{ N down } \quad 2$$

Force on top part of wire is

$$F_{\text{TOP}} = B_9 i l = \frac{4 \times 10^{-7}}{9 \times 10^{-2}} \times 5 \times 0.1$$
$$= 2.2 \times 10^{-6} \text{ N up. } \quad 2$$

So net force down =  $2.8 \times 10^{-6} \text{ N.}$  1

Force on side part of wire

$$dF = \frac{4 \times 10^{-7}}{y} i dy$$

$$\text{or } F = ~~20 \times 10^{-7}~~ 4 \times 10^{-7} \times i \int_{0.04}^{0.09} \frac{dy}{y} \quad 2$$

$$= 20 \times 10^{-7} \left[ \ln y \right]_{0.04}^{0.09}$$

$$= 20 \times 10^{-7} \ln \left( \frac{9}{4} \right)$$

$$= 1.62 \times 10^{-6} \text{ N to left. } \quad 2$$

5. When switch is turned to OFF, capacitor starts to be charged thru the 2 Megohm resistor.


P.D.  $V_c$  reached is

$$V = 12 \left( 1 - e^{-\frac{0.5}{1 \times 10^6 \times 2 \times 10^{-6}}} \right)$$


$$= 12 \left( 1 - e^{-0.5/2} \right)$$

$$= 12(1 - 0.78)$$

$$= 2.65 \text{ V}$$

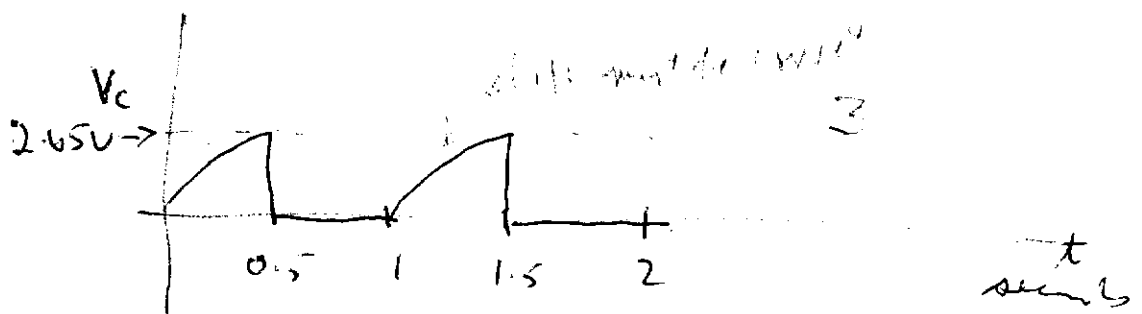

6.

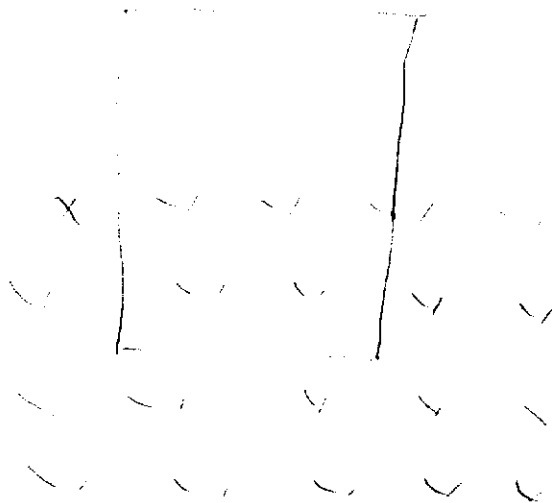

(a) When the force on the loop due to the magnetic field becomes equal to the weight, the net force and acceleration goes to zero.

6. When wire is fully out  $v$ .  $\mathcal{E} = B\omega v$ .

$$I = \frac{B\omega v}{R}$$

$$F = BIl = \frac{B^2 \omega^2 v}{R} = mg.$$

$$v = \frac{mgR}{B^2 \omega^2}$$

16